
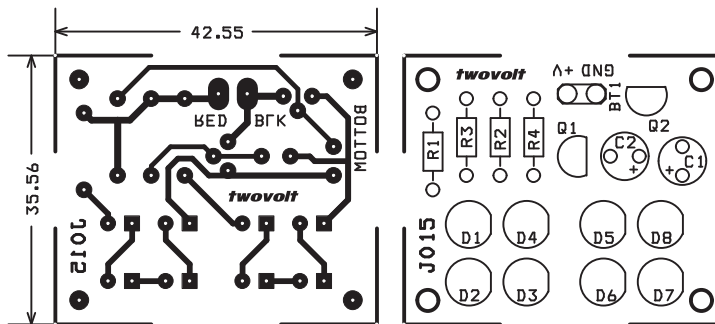


## 8 LED FLASHER

8 LED Flasher project simply flashes a set of 8 LED's to give you that reason to attract attention.

Power Supply : 9 V Battery (PP3)

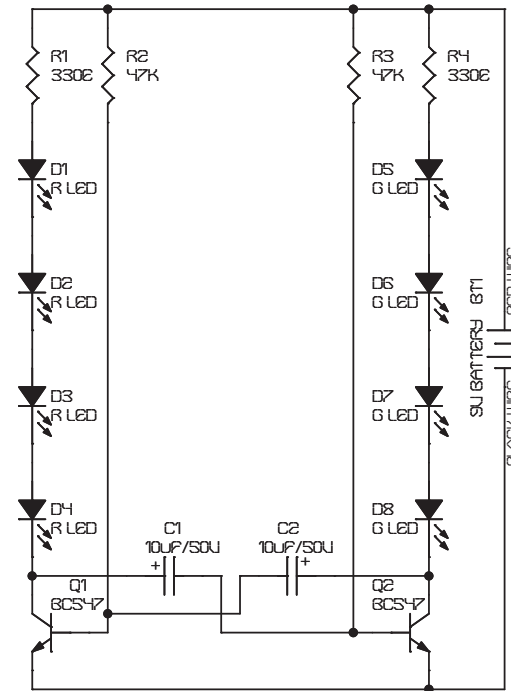

SR.	QTY.	REF.	DESCRIPTION
1	1	BT1	9V BATTERY SNAP
2	2	C1,C2	10uF/50V OR 63V
3	4	D1,D2,D3,D4	RED LED
4	4	D5,D6,D7,D8	GREEN LED
5	2	Q1,Q2	BC547
6	2	R1,R4	330E
7	2	R2,R3	47K