

LAMP FLASHER USING ATTINY85 ARDUINO COMPATIBLE

Lamp flasher using ATTINY85 micro-controller board, the project is Arduino compatible, simple code driver the entire circuit, circuit can lamp up to 500W, 230V AC. Timing of Flashes Can be adjusting by delay time in Arduino code.





